

(II) A 2.44-m-long coil containing 300 loops is wound on an iron core (average  $\mu = 2000\mu_0$ ) along with a second coil of 100 loops. The loops of each coil have a radius of 2.00-cm. If the current in the first coil drops uniformly from 12.0 A to zero in 98.0 ms, determine: (a) the mutual inductance  $M$ ; (b) the emf induced in the second coil.

(II) Determine the mutual inductance per unit length between two long solenoids, one inside the other, whose radii are  $r_1$  and  $r_2$  ( $r_2 < r_1$ ) and whose turns per unit length are  $n_1$  and  $n_2$ .

Compare the oscillations of an  $LRC$  circuit to the vibration of a mass  $m$  on a spring. What do  $L$  and  $C$  correspond to in the mechanical system?

(I) Estimate the inductance  $L$  of a 0.45-m-long air-filled coil 3.7 cm in diameter containing 20,000 loops.

(I) What is the inductance of a coil if it produces an emf of 8.50 V when the current in it changes uniformly from  $-22.0$  mA to  $+23.0$  mA in 21.0 ms?

Under what conditions is the impedance in an  $LRC$  circuit a minimum?


(I) How much energy is stored in a 400-mH inductor at an instant when the current is 9.0 A?

(II) It takes 2.56 ms for the current in an  $LR$  circuit to increase from zero to half its maximum value. Determine (a) the time constant of the circuit, (b) the resistance of the circuit if  $L = 310$  H.


(I) A 1.20-k $\Omega$  resistor and a 6.8- $\mu$ F capacitor are connected in series to an ac source. Calculate the impedance of the circuit if the source frequency is (a) 60 Hz; (b) 60,000 Hz.

(I) A 9.0-k $\Omega$  resistor is in series with a 26.0-mH inductor and an ac source. Calculate the impedance of the circuit if the source frequency is (a) 50 Hz; (b) 30,000 Hz.

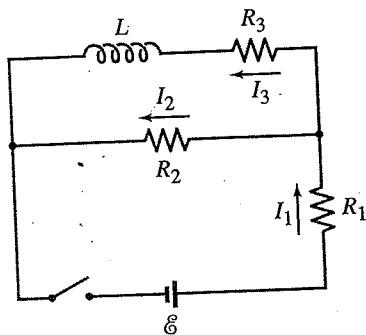(II) In the circuit of Fig. 30-16, determine the current in each resistor ( $I_1, I_2, I_3$ ) at the moment (a) the switch is closed, (b) a long time after the switch is closed. After the switch has been closed a long time, and reopened, what is each current (c) just after it is opened, (d) after a long time?



**Filter circuit.** The figure shows a simple filter circuit designed to pass dc voltages with minimal attenuation and to remove, as much as possible, any ac components (such as 60-Hz line voltage that could cause hum in a stereo receiver, for example). Assume  $V_{in} = V_1 + V_2$  where  $V_1$  is dc and  $V_2 = V_2 \sin \omega t$ , and that any resistance is very small. (a) Determine the current through the capacitor: give amplitude and phase (assume  $R = 0$  and  $X_L > X_C$ ). (b) Show that the ac component of the output voltage,  $V_{2 out}$ , equals  $Q/C$  where  $Q$  is the charge on the capacitor at any instant, and determine the amplitude and phase of  $V_{2 out}$ . (c) Show that the attenuation of the ac voltage is greatest when  $X_C \ll X_L$ , and calculate the ratio of the output to input ac voltage in this case. (d) Compare the dc output to input voltage.

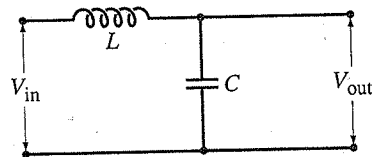

A pair of straight parallel thin wires, such as a lamp cord, each of radius  $r$ , are a distance  $l$  apart and carry current to a circuit some distance away. Ignoring the field within each wire, show that the inductance per unit length is  $(\mu_0/\pi) \ln[(l-r)/r]$ .