

1.

Physics 9C Winter 2016  
 Homework 7

$$\boxed{1} \text{ a) } \phi_B = N_2 A B_1 = N_2 A \frac{N_1 \mu_0 I_1}{l}$$

$\nearrow$  through loop 2      $\nearrow$   $A_1 = A_2$       $\nearrow$  due to loop 1      $B_1 = \frac{N_1 \mu_0 I_1}{l} = \frac{N_1 \mu_0 I_1}{l}$

$$M = N_1 N_2 \mu_0 A / l \quad \mu_0 \rightarrow \mu \text{ if iron core present}$$

$$= (300)(100) \frac{4\pi \cdot 10^{-7} (\pi) (0.02)^2 \cdot 2000}{2.44}$$

$$= .0388 \text{ Henries}$$

$$\text{b) } \mathcal{E} = M dI/dt = (.0388) \left( \frac{12}{.098} \right) = 4.75 \text{ volts}$$

$$\boxed{2} \text{ Solenoid: } \phi_B = LI = NA \mu_0 n I = \underbrace{N^2 A \mu_0 I}_{L}$$

$$L = (20000)^2 \pi (0.037/2)^2 4\pi \cdot 10^{-7} / .45$$

$$= 1.2 \text{ Henries}$$

$$\boxed{3} \quad \mathcal{E} = L dI/dt$$

$$8.5 = L \frac{45 \cdot 10^{-3}}{21 \cdot 10^{-3}} \Rightarrow L = 3.97 \text{ Henries}$$

2.

$$4) \text{ Energy} = \frac{1}{2} L I^2 = \frac{1}{2} (0.4)(9)^2 = 16.2 \text{ J}$$

$$5) \tau = L/R$$

$$\frac{1}{2} = e^{-t/\tau}$$

$$\ln \frac{1}{2} = -t/\tau$$

$$\ln 2 = t/\tau \quad \tau = \frac{t}{\ln 2} = \frac{2.56 \cdot 10^{-3}}{\ln 2}$$

$$= 0.00369 \text{ sec} = L/R$$

$$R = \frac{310}{0.00369} = 84 \text{ k}\Omega$$

6) Inductor tries to maintain current at previous value. since  $I_3 = 0$  before switch closed,  $I_3 = 0$  just after closed. Then  $I_1 = I_2$  and

$$I_1 = I_2 = \frac{\mathcal{E}}{R_1 + R_2} \quad \text{by kirchoff loop law}$$

b) after a long time, can treat inductor as resistors wire,  $I_1 = I_2 + I_3$

$$R_3 \quad \mathcal{E} - I_1 R_1 - I_2 R_2 = 0$$

$$\mathcal{E} - I_1 R_1 - (I_1 - I_2) R_3 = 0$$

$$R_2 \quad \mathcal{E} - I_1 (R_1 + R_3) + I_2 R_3 = 0$$

$$(R_3 + R_2) \mathcal{E} - I_1 (R_1 R_3 + R_1 R_2 + R_2 R_3) = 0$$

3.

$$I_1 = (R_2 + R_3) \epsilon / (R_1 R_2 + R_1 R_3 + R_2 R_3)$$

could also do by equivalent resistance method

$$R_2, R_3 \text{ in parallel} \Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = R_2 R_3 / (R_2 + R_3)$$

in series with  $R_1$ ,

$$I = \frac{\epsilon}{\left[ R_1 + R_2 R_3 / (R_2 + R_3) \right]}$$

$$= \epsilon (R_2 + R_3) / (R_1 R_2 + R_1 R_3 + R_2 R_3)$$


to get  $I_2, I_3$  use

$$I_2 = \frac{1}{R_2} (\epsilon - I_1 R_1)$$

$$\text{and } I_3 = I_1 - I_2$$

4.

7

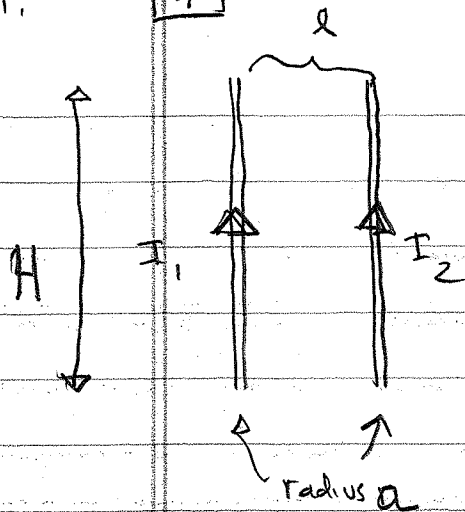

$$2\pi r B_1 = \mu_0 I_1 \quad \text{in region between wires}$$

$$\Phi_{B_1} = H \int_a^{l-a} \frac{\mu_0 I_1}{2\pi r} dr$$

length of  
wires

call radius "a"  
instead of r  
since like to  
use r for  
distance from wire

$$\frac{\Phi_{B_1}}{H} = \int_a^{l-a} \frac{\mu_0 I_1}{2\pi r} dr$$

flux per  
length

$$= \frac{\mu_0 I_1}{2\pi} \ln r \Big|_a^{l-a}$$

$$= \frac{\mu_0}{2\pi} \ln\left(\frac{l-a}{a}\right) I_1$$

inductance  
per length

same calculation for field due to  $I_2$  so final  
answer is

$$\frac{\mu_0}{\pi} \ln\left(\frac{l-a}{a}\right)$$

5.

8.

$$F = ma$$

← MASS ON spring



$$-kx - \gamma \frac{dx}{dt} = m \frac{d^2x}{dt^2}$$

$$m \frac{d^2x}{dt^2} + \gamma \frac{dx}{dt} + kx = 0$$

LRC circuit

$$Q/C + L \frac{dI}{dt} + IR = 0 \quad I = \frac{dQ}{dt}$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

$$m \frac{d^2x}{dt^2} + \gamma \frac{dx}{dt} + kx = 0$$

$$Q \leftrightarrow X$$

$$L \leftrightarrow m$$

$$R \leftrightarrow \gamma$$

$$1/C \leftrightarrow k$$